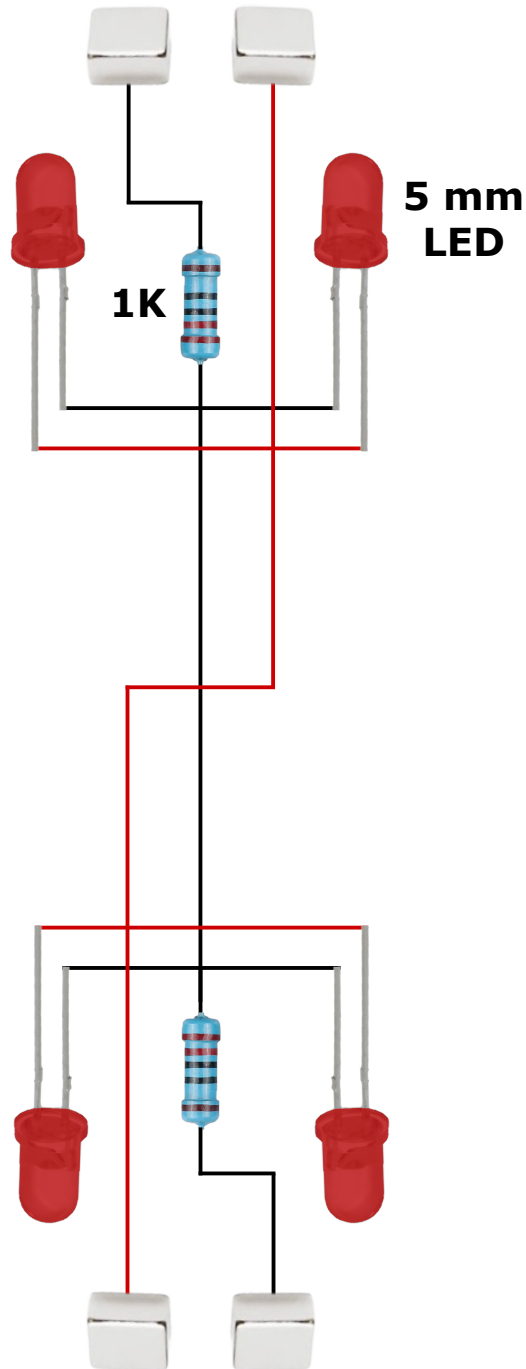


N52 5x5x3



Complexity	Number of connections	Type of circuit	Power consumption		
low	6	DC	113 milliwatts		
Notes The power consumption result is ideal. The connections are made using soldering wire. LED forward voltage: 2 V		Project title	Created by		
		Train Network	teoelectric		
		Drawing title	Drawing number		
		42			
			Rev.	Date of issue	Sheet
			-	-	1/1