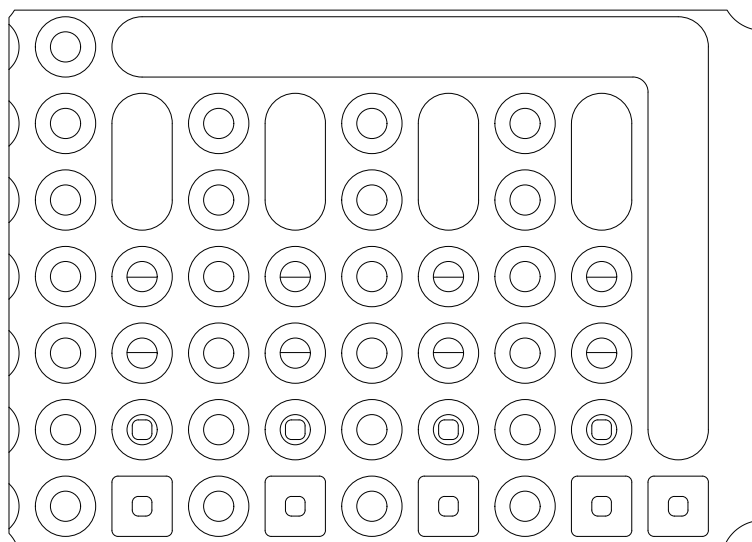
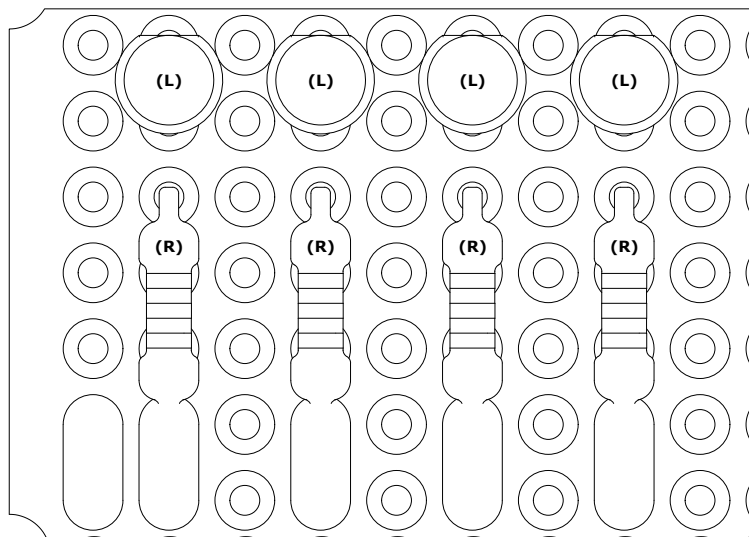




Complexity (Scale 0-5)	Number of components	Type of circuit (Power Supply: 5V)	Power consumption		
Level 3	8	Direct Current	0.04 watts		
Notes The connections are made using soldering wire. PCB slots number 9 x 7 Resistors (R) value: 1K LEDs (L) $V_F \approx 3\text{ V}$		Project title	Created by		
		Sunflower Display Wiring Diagram	teolectric		
			Drawing number		
			Rev.	Date of issue	Sheet
			B	18/11/2025	1/1
			10		